

Student Name : _____ Stuc _____



	Max Mark	Student Mark
Problem 1	45	
Problem 2	20	
Problem 3	20	
Problem 4	15	
Sum	100	

Problem 1 Solution(45 pts)

1	2	3
C	D	C
4	5	6
D	D	C
7	8	9
B	B	C
10	11	12
E	C	B
13	14	15
A	B	C

Problem 1 Solution(45 pts)

Please fill the Answer in the table shown in the first sheet . (3 Point each)

1. The design flow of IC design system is :

1. architecture design 2. market requirement 3. Layout 4. HDL coding 5. logic design

A. 5-1-2-4-3

B. 2-1-5-3-4

C. 2-1-5-4-3

D. 4-1-3-2-5

E. 5-3-2-1-4

2. CMOS NANS gate is better than CMOS NOR gates because

A. CMOS nor takes more space than NAND

B. CMOS NOR uses P channel transistor in parallel.

C. CMOS NAND uses P channel transistor in parallel.

D. Only A and C is correct.

E. All (A and B and C) are correct

3. How many transistors are required to implement a four-input OR using CMOS design style?

A. 6

B. 8

C. 10

D. 12

E. None

4. In order to have "pass" logic gate We need

A. An N-channel and P-Channel transistor in series

B. We need only p-channel so it will pass good one.

C. We need only N-channel so it will pass good zero.

D. An N-channel and P-Channel transistor in parallel

E. None

5. For the circuit in Fig. below, determine the final value of V_A , V_B , V_C , assuming initial condition at each of the nodes is 3V and $V_{TP} = -0.5V$ (ignore body effect).


A. $V_A = 3V$ $V_B = 2V$ $V_C = 1.5V$

B. $V_A = 1.5V$ $V_B = 1.5V$ $V_C = 1.5V$


C. $V_A = 2V$ $V_B = 2V$ $V_C = 2V$

D. $V_A = 1.5V$ $V_B = 2V$ $V_C = 2V$

E. None

 

 
6. Assuming that switch as shown in figure below closes at time $t = 0$, what is the output voltage at $t = 0+$ and $t = \infty$? C_L was initially discharged, $V_{TP} = -0.5V$.
- $V_{out}(t = 0+) = +1V$ $V_{out}(t = \infty) = -1.5V$
 - $V_{out}(t = 0+) = -1V$ $V_{out}(t = \infty) = +1.5V$
 - $V_{out}(t = 0+) = -1V$ $V_{out}(t = \infty) = -1.5V$**
 - $V_{out}(t = 0+) = +1V$ $V_{out}(t = \infty) = +1.5V$
 - None



7. The delay of a static CMOS inverter is minimized if $(W/L)_p / (W/L)_n = \mu_n / \mu_p$.
- True
 - False**
 - None
8. The load capacitance of a static CMOS gate has no effect on its VTC
- False
 - True**
 - None
9. ----- connects between 2 segments of metal layers
- Contact
 - Poly
 - Via**
 - Diffusion
 - None
10. CMOS Transmission (Pass) Gates , capable of passing both '1' and '0'
- Good "1"
 - Good "0"
 - Poor "1"
 - Poor "0"
 - Both A and B only**

11. What is the logic function performed by this circuit?

 - A. The circuit is a NOR gate.
- B. The circuit is a XOR gate.
- C. The circuit is a NAND gate.**
- D. The circuit is a NOT gate.
- E. None



12. Increasing power supply voltage, V_{DD} , will

- A. Does not change the speed performance of CMOS gates.
- B. Increase the speed performance of CMOS gates.**
- C. Decrease the speed performance of CMOS gates.
- D. None

13. The IN and OUT bus lines in IC design should be in

- A. Metal**
- B. Contact
- C. Polysilicon
- D. Diffusion
- E. Silicon
- F. None

14. If an NMOSFET gate's dielectric were changed from SiO_2 to a low-K material with half the permittivity of SiO_2 , what would happen to its I_D ? You may assume that $V_{GS} \geq V_{TN}$

- A. I_D does not change.
- B. I_D being halved.**
- C. I_D doubled.
- D. I_D does not change.**
- E. None

15. Which one is the right order for the following the following interconnect fabrication steps :

- Etch metal. • Expose photoresist using mask. • Remove all photoresist.
 - Deposit photoresist. • Deposit metal everywhere.
- A. 1) Deposit metal everywhere. 2) Expose photoresist using mask. 3) Deposit photoresist 4) Etch metal. 5) Remove all photoresist
 - B. 1) Deposit photoresist 2) Deposit metal everywhere 3) Expose photoresist using mask. 4) Etch metal. 5) Remove all photoresist
 - C. 1) Deposit metal everywhere. 2) Deposit photoresist. 3) Expose photoresist using mask. 4) Etch metal. 5) Remove all photoresist**
 - D. 1) Deposit metal everywhere. 2) Expose photoresist using mask. 3) Deposit photoresist. 4) Etch metal. 5) Remove all photoresist
 - E. None

IC Design ENCS333

Midterm Jun-16-2023

Student Name : _____ Stuc _____




Problem 2: (20 pts)

- A. Consider an N-channel MOSFET. You may assume that this MOSFET has no oxide charge. Fill in the blank cells in the table, using the following symbols: \uparrow for increase, \downarrow for decrease, and \rightarrow for no change. If the cell has already been provided with an X it means that you are not responsible for filling that cell out. When moving along a row consider only the change brought on due to the parameter specified in the first cell of that row. (7 pts)

	V_t	V_{FB}	μ_s	I_{ds}
$T_{ox} \uparrow$	increase	No change	Assume V_t is unchanged increase	Assume μ_s remains unchanged decreases
Temperature \uparrow	X	decreases	decrease	Assume V_t is constant and decrease

- B. Answer the following Questions about the figure shown below : (13 pts)


- What does this layout represent ? _____
- How many contacts does it Have ? _____
- How Many Poly head/contact it has ? _____
- Mark the length(L_n) and the width (w_p , w_n) of devices on the figure
- Sketch the equivalent detail schematic and the schematic symbol view.

 


Problem 3: (20 pts)

1. Indicate the regions of operation of the transistors shown in the circuits in the tables next to the circuits. Assume short channel devices unless otherwise stated $V_{Tn}=V_{Tp}= 0.3\text{ V}$, $V_{vsatn}= 0.3\text{ V}$, $V_{vsatp}= 0.6\text{ V}$ and neglect the body effect. **(10 pts)**


Solutions:

 

Voltage IN	Region of Operation	
	M1	M2
GND (0 V)	O cutoff	X cutoff
	O linear	O linear
	X saturation	O saturation
	O vel. saturation	O vel. saturation
VDD (1.2 V)	X cutoff	O cutoff
	O linear	O linear
	O saturation	X saturation
	O vel. saturation	O vel. saturation

 


Region of Operation	
M1	M2
O cutoff	O cutoff
X linear	O linear
O saturation	X saturation

 


IN	M1	M2
GND (0 V)	X cutoff	O cutoff
	O linear	X linear
	O saturation	O saturation
	O vel. saturation	O vel. saturation
VDD (1.2 V)	O cutoff	X cutoff
	X linear	O linear
	O saturation	O saturation
	O vel. saturation	O vel. saturation

 2. Consider the And-OR-Inverter (AOI) cell shown in Figure below. Derive the CMOS complex gate that implements this cell with minimum number of transistors. (5 pts)



Solutions:

 

$$T1 = X_1.X_2$$

$$T2 = X_3.X_4$$

Pull-Up Network

$$F = (X_1.X_2 + X_3.X_4 + X_5)'$$

$$F = (X_1' + X_2') (X_3' + X_4').X_5'$$

$$F =$$

$$(X_1'X_3' + X_1'X_4' + X_2'X_3' + X_2'X_4')X_5'$$

Pull-Down Network

$$F = (X_1.X_2) + (X_3.X_4) + X_5'$$


3. Consider the layout in Figure below (5 pts)

(a) What type of logic function does this layout implement?

A messed up inverter.

(b) Point out the three largest problems with this layout. For each explain the impact on gate behavior. When possible, indicate the ways in which important parameters are influenced, e.g., k_0 .

 - i. The bottom half of the NMOSFET gate is missing.
- ii. The PMOSFET drain is bigger than it needs to be, increasing capacitance without benefit.
- iii. The NMOSFET and PMOSFET active regions are the same width, which would result in asymmetric pull-up and pull-down resistances if the gates were designed correctly.




Student Name : _____ Stuc _____

Problem 3: (15 pts)

- Implement the following function as a single logic gate. Indicate the widths of all gates in terms of k , the minimal gate width. Size the transistors to achieve the same worst-case resistance as a balanced, minimal width inverter (i.e., an inverter with a w -wide NMOSFET and a $2k$ -wide PMOSFET). (5 pts)

$$f(a, b, c, d) = a'(bc' + d)$$

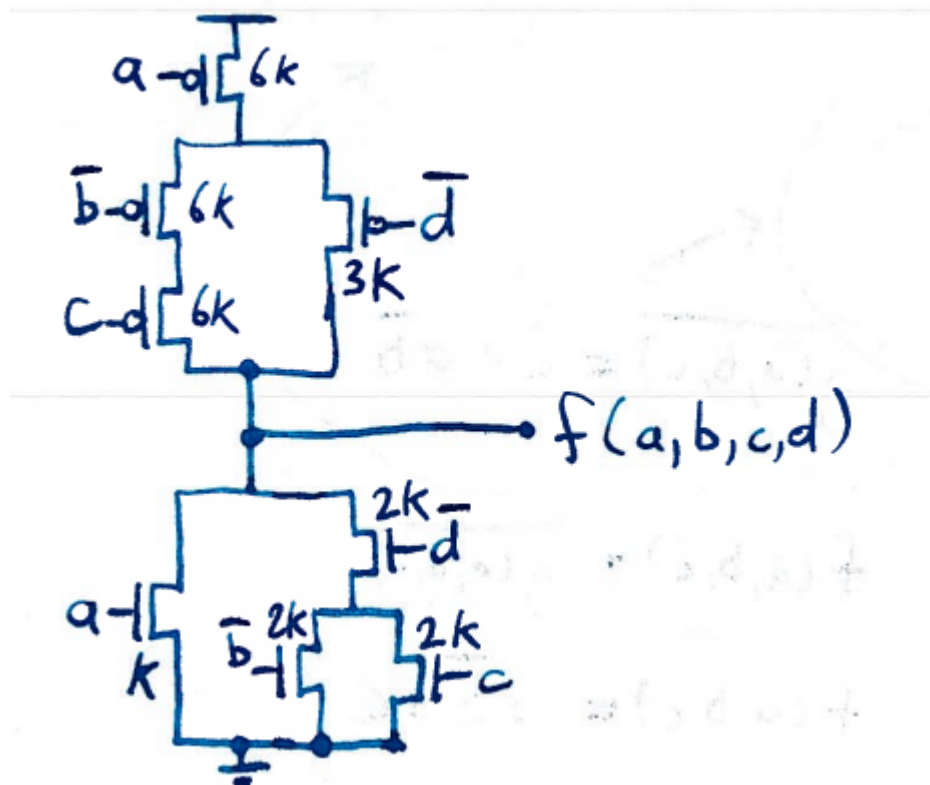

- Implement the following function using the minimal number of transistors. The output of your implementation should have full output range, from VSS to VDD. However, it needn't be particularly fast or can have weak signal at some stages. You may use literals as direct inputs. (5 pts)

$$f(a, b, c) = (ab' + a'b)c$$

Most or full credit was given for same designs w. ≤ 8 transistors. However, I wanted to see how far this could be pushed.

